

Student 1 Roll No. \_\_\_\_\_

Evaluator 1 Roll No. \_\_\_\_\_

Student 2 Roll No. \_\_\_\_\_

Evaluator 2 Roll No. \_\_\_\_\_

**Problem 1 (40 Marks)**

For the initial value problem:


$$y'' + 4y' + 4y = e^{-2t} \sin 2t,$$

$$y(0) = 1 \text{ and } y'(0) = -1.5$$

- Determine whether the system is stable, unstable or marginally stable.
- Find value of natural frequency ( $\omega_o$ ), damping ratio ( $\zeta$ ) and quality factor ( $Q$ ).
- Is the system undamped, underdamped, overdamped or critically damped?
- Solve the initial value problem.

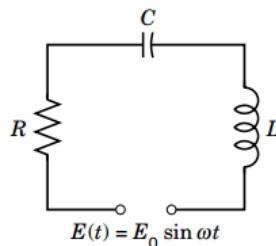**Problem 2 (40 Marks)**

Consider the initial value problem for the RLC circuit given in the following figure. The data is given as:  $R=8$ ,  $L=0.2$ ,  $C=0.0125$ ,  $E=100\cos 10t$ . Assume zero initial current and initial charge.



- Determine whether the system is stable, unstable or marginally stable.
- Find value of natural frequency ( $\omega_o$ ), damping ratio ( $\zeta$ ) and quality factor ( $Q$ ).
- Is the system undamped, underdamped, overdamped or critically damped?
- Solve the initial value problem.